

ECE 551

HW4 *(100 pts)*

-
- Due Weds Nov 6th at class
 - Work Individually
 - Use descriptive signal names
 - Comment & indent your code
 - Code will be judged on coding style

HW4 Problems 1&2 (10pts) + (10pts)

1. **(10pts)** Complete the Synopsys Design Vision tutorial. Sign below, (preferably in blood).

I, Dylan Clark completed the Synopsys Design Vision tutorial. If I had any problems with it, I discussed them with the TA or Instructor, either in person, or through email.

2. **(10pts)** Project Team Formation

Form a 3 or 4 person project team, **Come up with a team name**, and fill in the table below:

Team Name:	Moore's Are For Wh***s
Person1:	Zach Chanak
Person2:	Aksei Torgerson
Person3:	Dylan Clark
Person4:	

HW4 Problem 3 (20pts) Synthesize your telemetry.v


This problem started as Ex14 on Weds Oct 30th

- In HW3 you produced the telemetry module (**telemetry.v**) which instantiated **UART_tx.v** (**NOTE:** if your **telemetry.v** code is a big ball of stink, and one of your project partners has a better **telemetry** you can use their code. You **still** have to do the synthesis **individually**)
- In this HW you will synthesize **telemetry** using Synopsys on the CAE linux machines.
- Write a synthesis script to synthesize your telemetry. The script should perform the following:
 - Defines a clock of 500MHz frequency and sources it to clock
 - Performs a set don't touch on the clock network
 - Defines input delays of 0.5 ns on all inputs other than clock
 - Defines a drive strength equivalent to a 2-input nand of size 1 from the Synopsys 32nm library (NAND2X1_RVT) for all inputs except clock and rst_n
 - Defines an output delay of 0.75ns on all outputs.
 - Defines a 0.15pf load on all outputs.
 - Sets a max transition time of 0.15ns on all nodes.
 - Employs the Synopsys 32nm wire load model for a block of size 16000 sq microns
 - Compiles, then flattens the design so it has no hierarchy, and compiles again.
 - Produces a min_delay report
 - Produces a max_delay report
 - Produces an area report
 - Flattens the design so it has no hierarchy
 - Writes out the gate level verilog netlist (**telemetry.vg**)
- Submit to the dropbox.
 - Your synthesis script (**telemetry.dc**)
 - The output reports for area (**telemetry_area.txt**)
 - The gate level verilog netlist (**telemetry.vg**)

HW4 Problem 4 (20pts) brushless.sv

This problem started as Ex12 on Weds Oct 23rd


- Do you remember anything of what you learned back in HW1 about how a brushless DC motor is driven?
- There are 3 coil connections that we have to drive. We call them green, yellow, and blue. For any given coil we drive current in one direction, the opposite direction, or not at all.
- How do we know the proper coil drive at any given time? That is determined by the position of the rotor. We know the rotor position from the hall sensor inputs.

 

- **brushless.sv** will be the block that inspects the hall sensor signals and determines how to drive each coil. Each coil can be driven 1 of 4 ways: not driven (both high/low FETs off); driven "forward"; driven "reverse"; driven for dynamic braking (high FET off, low FET PWMed)
- Are the hall effect sensors synchronous to our clock domain? What does that mean?
- If you are curious why PWMing the lower FETs creates dynamic braking I think I can stumble through an explanation, but I suspect most of you lemmings will be content to just implement it as specified.

HW4 Problem 4 (20pts) brushless.sv

 This problem started as Ex12 on Weds Oct 23rd



18V will be considered “virtual ground” for the coils. Thus our FETs allow us to drive positive or negative.

The use of PWM allows us to control the effective magnitude of the voltage applied across the coil. (hence speed/torque)

A PWM setting of 0x400 would be 50% and would represent driving a coil with 18V (virtual ground).

There are 4 possible states a coil can be driven in. Regenerative braking is a special case indicated by **brake_n** signal being low.

Coil Drive State:	FET gate controls:
Not driven (High Z)	Both high and low side low (both off)
Forward Current	High side driven with PWM, low side driven with ~PWM
Reverse Current	High side driven with ~PWM, low side driven with PWM
Regen Braking	High side low (off), low side driven with PWM

HW4 Problem 4 (20pts) brushless.sv

Determining next drive conditions from hall effect sensor readings:

- The hall effect sensors tell us the current position of the rotor
- The hall effect sensor wires are also green, yellow, and blue.
- Form a 3-bit vector: **rotation_state = {hallGrn,hallYlw,hallBlu};**
- The following table outlines how we drive our coils

rotation_state	3'b101	3'b100	3'b110	3'b010	3'b011	3'b001
coilGrn	for_curr	for_curr	High Z	rev_curr	rev_curr	High Z
coilYlw	rev_curr	High Z	for_curr	for_curr	High Z	rev_cur
coilBlu	High Z	rev_curr	rev_curr	High Z	for_curr	for_curr

- In the case of **brake_n == 1'b0** (braking) all coils are driven in the regenerative braking state with the high side FET off and the low side FET PWMing.

HW4 Problem 4 (20pts) brushless.sv

Signal:	Dir:	Description:
clk,rst_n	in	50MHz clock & active low reset
drv_mag[11:0]	in	From PID control. How much motor assists (unsigned)
hallGrn,hallYlw, hallBlu	in	Raw hall effect sensors (asynch)
brake_n	in	If low activate regenerative braking at 75% duty cycle
duty[10:0]	out	Duty cycle to be used for PWM inside <i>mtr_drv</i> . Should be 0x400+drv_mag[11:2] in normal operation and 0x600 if braking.
selGrn[1:0], selYlw[1:0], selBlu[1:0]	out	2-bit vectors directing how <i>mtr_drv</i> should drive the FETs. 00=>HIGH_Z, 01=>for_curr, 10=>rev_curr, 11=>regen braking

Code and test ***brushless.sv*** with the interface specified in this table.


Submit: **brushless.sv** and **brushless_tb.sv**. I will let you get away with a rather cheesy incomplete test bench this time since we will test this on the demo platform.

This problem started as Ex13 on Mon Oct 28th


HW4 Problem 5 (15pts) mtr_drv.sv

- Back in HW3 you produced both **PWM11.sv** and **nonoverlap.sv**. This block is a simple combination of these to produce **mtr_drv.sv**

 
- Coils can be driven 1 of 4 ways:
 - Not driven (high impedance)
 - Reverse current (\sim PWM_sig/PWM_sig)
 - Forward current (PWM_sig/ \sim PWM_sig)
 - Dynamic braking (0 for high side, PWM for low side)



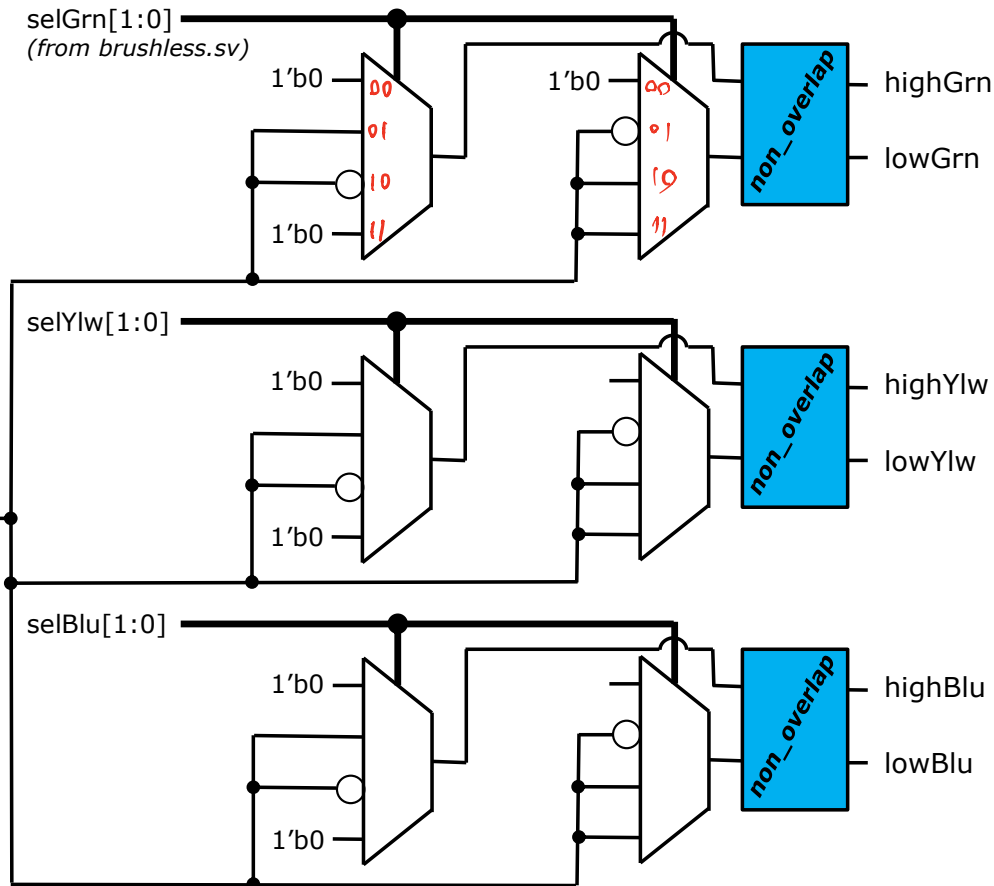
- Code and test what you see here. (**clk** and **rst_n** are not shown, but obviously part of this block and almost everything we do)
- Submit **mtr_drv.sv** and **mtr_drv_tb.sv**.



 HW4 Problem 6 (25pts) Testing **brushless** & **mtr_drv** on platform



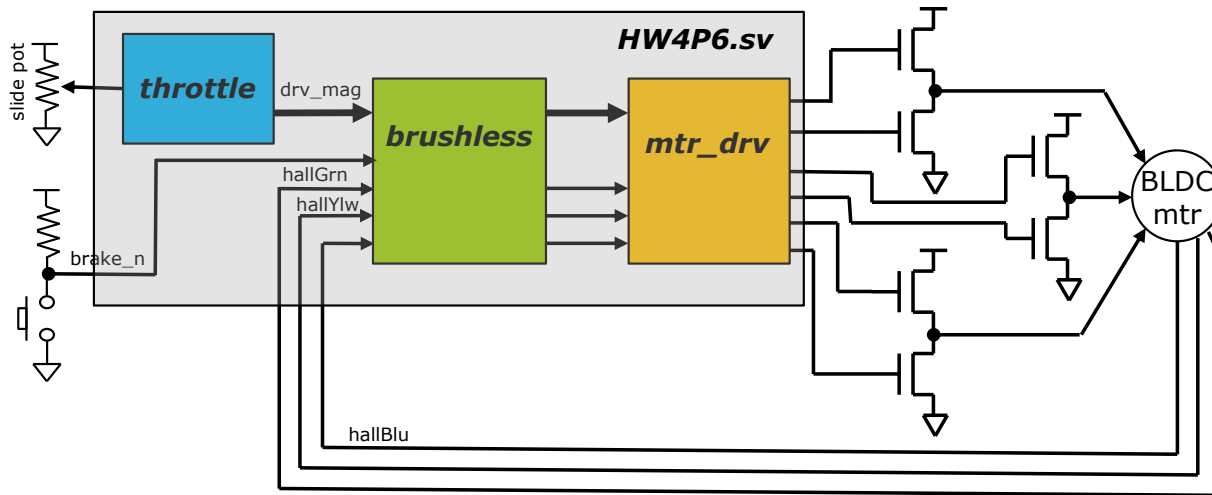HW4 Problem 6 (25pts) Testing **brushless** & **mtr_drv** on platform



- For this problem you will map your **brushless** and **mtr_drv** designs to a FPGA that exists on the test platform, and test that they function properly by driving a ebike hub motor (BLDC mtr).
- The code to interface to the slide potentiometer (that serves as a throttle) is provided (**throttle.sv**). The shell to wrap things together **HW4P6.sv** is also provided.
- Download the provided .sv files along with **HW4P6.qpf** and **HW4P6.qsf**. Launch Quartus using the provided .qpf. Compile and map to the DE-0 on the test platform.
- Submit a video showing you download the code to the DE-0 and running the motor **at various speeds**. End the video with a push of the brake button. Include a shot of **your face** in the video (helps me associate names with faces).

rotation_state	3'b101	3'b100	3'b110	3'b010	3'b011	3'b001
coilGrn	for_curr	for_curr	High Z	rev_curr	rev_curr	High Z
coilYlw	rev_curr	High Z	for_curr	for_curr	High Z	rev_curr
coilBlu	High Z	rev_curr	rev_curr	High Z	for_curr	for_curr

- In the case of **brake_n == 1'b0** (braking) all regenerative braking state with the high side FET PWMing.

Coils can be driven 1 of 4 ways:

- Not driven (high impedance)
- Reverse current (~PWM_sig/PWM_sig)
- Forward current (PWM_sig/~PWM_sig)
- Dynamic braking (0 for high side, PWM for low side)

6

101 :	highGrn	lowGrn	highYlw	lowYlw	highBlu	lowBlu
Expected	PWM	$\overline{\text{PWM}}$	$\overline{\text{PWM}}$	PWM	0	0
1	1	0	0	0	0	1
0	0	1	1	X	0	0

100 :	highGrn	lowGrn	highYlw	lowYlw	highBlu	lowBlu
	PWM	$\overline{\text{PWM}}$	0	0	$\overline{\text{PWM}}$	PWM
0	0	1	0	0	1	X
1	1	0	0	X	0	X

110 :	highGrn	lowGrn	highYlw	lowYlw	highBlu	lowBlu
	0	0	PWM	$\overline{\text{PWM}}$	$\overline{\text{PWM}}$	PWM
1	0	X	1	0	0	X
0	0	0	0	1	1	X
1	0	X	1	0	0	X

again? 010 :	highGrn	lowGrn	highYlw	lowYlw	highBlu	lowBlu
	$\overline{\text{PWM}}$	PWM	PWM	$\overline{\text{PWM}}$	0	0
1	0	X	1	0	0	X
0	1	X	0	1	0	0

011 :		highGrn	lowGrn	highYlw	lowYlw	highBlu	lowBlu
		\overline{Pwm}	Pwm	0	0	Pwm	\overline{Pwm}
0	1	1	X	0	0	0	1
1		0	0	0	X	1	0

001 :		highGrn	lowGrn	highYlw	lowYlw	highBlu	lowBlu
		0	0	\overline{Pwm}	Pwm	Pwm	\overline{Pwm}
1		0	X	0	0	1	0
0		0	0	1	X	0	1

000 :		highGrn	lowGrn	highYlw	lowYlw	highBlu	lowBlu
		0	0	0	0	0	0
$Pwm = 1$		0	1	0	1	0	1
0		0	0	0	0	0	0

111 :		highGrn	lowGrn	highYlw	lowYlw	highBlu	lowBlu
		0	1	0	1	0	1
$Pwm = 1$							
0							